



# Finding Maximum Number Using Array Structure

By Prawat Nagvajara

 


Fig. 1 Maximum Number Finder Array (max\_array) Comprises Processing Elements

## Synopsis

An implementation on FPGA - an array structure that outputs the maximum N-bit unsigned number out of L input n-bit unsigned numbers.

Figure 1 shows a schematic where L numbers are the N-bit chunks of the inputs x : in `std_logic_vector(N*L - 1 downto 0)`; and the out z: out `std_logic_vector(N-1 downto 0)` is the maximum.

The Processing Element – PE each compares the two inputs x and y, and multiplexes out the greater, that is, if  $x > y$  then  $z \leq x$ ; else  $z \leq y$ ; end if; (Fig. 2). The number zero, 0 (an input to the leftmost PE in Fig. 1), is a vector of all '0'. The VHDL syntax is (others => '0'). The array structure propagates the maximum out to the output z.



Fig. 2 Processing Element

## Algorithm

The array implements the following algorithm. The max\_unsigned function takes as the inputs  $N*L$  -bit vector where  $x(N*i + N-1 \text{ downto } n*i)$ ,  $0 \leq i \leq L-1$  is the  $i$ th N-bit unsigned, and outputs the maximum.

```
-----
-- max_unsigned function
-- Input x: L N-bit unsigned
-- Initialize temp to 0, iteratively
-- compare each number to temp and
-- update temp as a current maximum
-----

function max_unsigned
(x:std_logic_vector; L, N: natural)
return std_logic_vector is
variable temp:
  std_logic_vector(N-1 downto 0)
:= (others => '0');
begin
  for i in L-1 downto 0 loop
    if unsigned (x(N*i + N-1 downto N*i))
      > unsigned (temp) then
      temp := x(N*i + N-1 downto N*i);
    end if;
  end loop;
  return temp;
end function max_unsigned;
```

## Code

VHDL code of the PE (below) uses the IEEE std\_logic\_arith and the std\_logic\_unsigned packages to output the maximum number. The inputs x and y are cast to unsigned. If the problem were signed numbers cast x and y to signed .

```
-----
-- Company: Drexel ECE
-- Engineer: Pravat
-- Array of N processing elements
-- returns maximum number out of N unsigned numbers
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
Use IEEE.STD_LOGIC_ARITH.all, IEEE.STD_LOGIC_UNSIGNED.all;
entity pe is
generic(n: natural := 8);
  Port (x, y : in std_logic_vector(n-1 downto 0);
        z : out std_logic_vector(n-1 downto 0)
  );
end pe;
architecture Beh of pe is
begin
  process(x, y)
  begin
    if unsigned(x) > unsigned(y) then
      z <= x;
    else
      z <= y;
    end if;
  end process;
end beh;
```

The max\_array entity below consists of the processing elements connected by the signal w(i), i = L-1, ..., 0. (Fig. 1) and. w(L-1) is assigned to 0, i.e., (others => '0').

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity max_array is
generic(L: natural := 10;
       N: natural := 8);
  Port (x: in std_logic_vector(N*L - 1 downto 0);
        z: out std_logic_vector(N-1 downto 0)
  );
end max_array;

architecture struc of max_array is
type vector_array is array (natural range <>) of
std_logic_vector(n-1 downto 0);
signal w: vector_array(L-1 downto 0);
component pe
generic(n: natural := 8);
  Port (x, y : in std_logic_vector(n-1 downto 0);
        z : out std_logic_vector(n-1 downto 0)
  );
end component;
```

```
begin

w(L-1) <= (others => '0');

G1: for i in L-1 downto 0 generate
  G2: if i > 0 generate
    cell: pe generic map(N)
    port map(w(i), x(N*i+N-1 downto N*i),w(i-1));
  end generate G2;
  G3: if i = 0 generate
    cell: pe generic map(N)
    port map(w(i), x(N*i + N-1 downto N*i),z);
  end generate G3;
end generate G1;
end struc;
```

An instance of max\_array with L = 5 numbers and N = 3, 3-bit number ranges from 0 to 7. The input vector x is L\*N = 15 bits makes up the five 3-bits chunks.

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity max_array_5x3 is
  Port (x: in std_logic_vector(14 downto 0);
        z: out std_logic_vector(2 downto 0)
  );
end max_array_5x3;

architecture struc of max_array_5x3 is

component max_array
generic(L: natural := 10;
       N: natural := 8);
  Port (x: in std_logic_vector(N*L - 1 downto 0);
        z: out std_logic_vector(N-1 downto 0)
  );
end component;

begin
U1: max_array generic map(5, 3)
port map (x, z);
end struc;
```

## Exercises

Reader can experiment with a signed maximum finder, where the smallest N-bit number is -2N-1, i.e., (2\*\*(N-1) => '1', others => '0') in VHDL syntax.

Reader can design an array sorter using L rows of a modified max\_array whose processing elements sort the maximum and minimum of the two inputs. The number l inputs of the ith row reduces, l = L-i, i=0, ..., L-1, as each row finds the maximum. The L outputs are the sorted list of the L numbers.