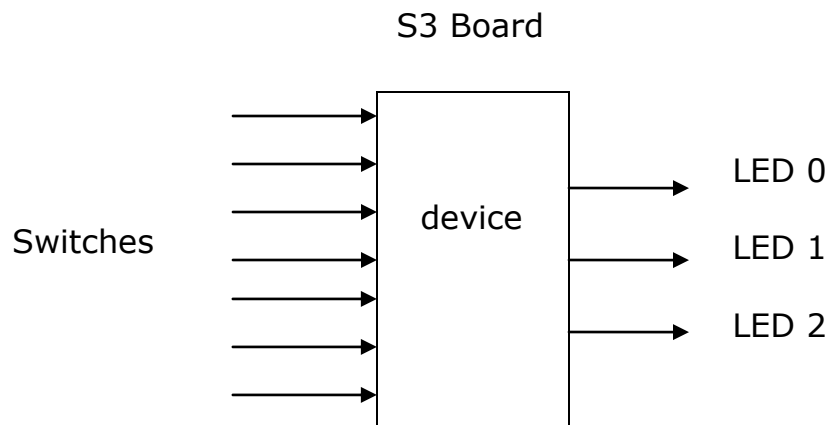




Electrical and Computer Engineering
ECE-C302

Quiz 1

Implement a 7-inputs and 3-outputs device. The outputs are a binary vector representing the number of one's appearing at the input ports ranges from 0 to 7.



Solution

Entity device is

```
Port (x : in std_logic_vector(0 to 6);  
      Z: out std_logic_vector(2 downto 0));  
End device;
```

Architecture beh of device is

```
Begin  
Process(x)  
Variable count : integer;  
Begin  
Count := 0;  
For I in 0 to 6 loop  
    If x(i) = '1' then count := count + 1; end if;  
End loop;  
Case count is
```

```
When 0 => z <= "000";  
When 1 => Z <= "001";  
When 2 => z <= "010";  
When 3 => Z <= "011";  
When 4 => z <= "100";  
When 5 => Z <= "101";  
When 6 => z <= "110";  
When 7 => Z <= "111";  
When others => null;  
End case;  
End process;
```