



Synopsis

This note covers three design problems on register buffers: Parallel to Serial Buffer, Serial to Parallel Buffer and Double Buffer. Problem 3 shows an implementation on FPGA.

Problem 1 Parallel-in Serial-out Register

 


Fig. 1.1 Parallel-in Serial-out Shift Register

```
-----  
-- Company: Drexel ECE  
-- Engineer: Prawat  
-- parallel-in serial-out register  
-- After reset the register loads new data,  
-- then shifts the n bits content out.  
-- Once the leftmost bit at output,  
-- the register loads the new data.  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
  
entity p2s is  
generic (n : natural := 2);  
port (ck, reset : in std_logic;  
      x: in std_logic_vector(n-1 downto 0);  
      z: out std_logic);  
end p2s;
```

```

architecture Behavioral of p2s is
  signal temp : std_logic_vector(n-1 downto 0);
begin
  z <= temp(0); -- wire output
  process(ck)
    subtype my_int is integer range 0 to n-1;
    variable count : my_int;
  begin
    if ck='1' and ck'event then
      if reset = '1' then temp <= x; count := 0; else
        if count < n-1 then
          temp <= '0' & temp(n-1 downto 1);
          count := count + 1;
        else
          temp <= x; count := 0;
        end if;
      end if;
    end if;
  end process;
end Behavioral;

```

 


Fig. 1.2 Simulation Wave

Problem 2 Serial-in parallel-out register

 


Fig. 2.1 Serial-in Parallel-out Register

```
-----
-- Company: Drexel ECE
-- Engineer: Prawat
-- serial-in parallel-out register
-- After reset the register loads a new bit
-- by right-shifting the content of temp1.
-- After n loads and temp2 <= temp1;
-- In this fashion, the circuit chunks bit
-- serial into a string of n-bit vectors.
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity s2p is
generic (n : natural := 2);
port (x, ck, reset : in std_logic;
      z: out std_logic_vector(n-1 downto 0)
);
end s2p;
```

```

architecture Behavioral of s2p is
signal temp1, temp2 :
    std_logic_vector(n-1 downto 0);
begin
z <= temp2;-- wire output
process(ck)
subtype my_int is integer range 0 to n;
variable count : my_int;
begin
if ck='1' and ck'event then
    if reset = '1' then
        temp1 <= (others => '0');
        temp2 <= (others => '0');
        count := 0; else
        if count < n then
            temp1 <= x&temp1(n-1 downto 1);
            count := count + 1;
        else
            -- shift and chunk to temp2
            temp1 <= x&temp1(n-1 downto 1);
            temp2 <= temp1;
            -- one already one shift
            count := 1;
        end if;
    end if;
end if;
end process;
end Behavioral;

```

 


Fig. 2.2 Simulation Wave

Problem 3 Double buffer



Fig. 3 Double Buffer

```

-----
-- Company: Drexel ECE
-- Engineer: Prawat
-- Double buffers: shift registers temp1, temp2
-- Two-state state machine. The states are
-- in_temp1_out_temp2, in_temp2_out_temp1
-- the state toggles as buffered register filled
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity double_buffer is
generic(n : natural);
port (ck, reset : in std_logic;
      x: in std_logic;
      z: out std_logic;
      z1: out std_logic_vector(n-1 downto 0);
      z2: out std_logic_vector(n-1 downto 0);
      t1, t2: out std_logic);
end double_buffer;

architecture Behavioral of double_buffer is
signal temp1, temp2 : std_logic_vector(n-1 downto 0);
type my_state is (in_temp1_out_temp2, in_temp2_out_temp1);
signal n_s: my_state;
signal sel: std_logic; -- output mux select

begin
  -----
  -- debug signals to LEDs
  -----

  z1 <= temp1; z2 <= temp2; -- buffer contents
  t1 <= sel; t2 <= not sel; -- present state
  -----

```

```

process(ck)
variable count : integer;
begin
  if ck='1' and ck'event then
    if reset = '1' then
      n_s <= in_temp1_out_temp2;
      temp1 <= (others => '0');
      temp2 <= (others => '0');
      sel <= '0'; count := 0; else
        case n_s is
          when in_temp1_out_temp2 =>
            temp1 <= x&temp1(n-1 downto 1);
            temp2 <= '0'&temp2(n-1 downto 1);
            if count = n-1 then
              n_s <= in_temp2_out_temp1;
              sel <= '1'; -- mux temp1(0) to output
              count := 0;
            else
              sel <= '0'; -- mux temp2(0) to output
              count := count + 1;
            end if;
          when in_temp2_out_temp1 =>
            temp2 <= x&temp2(n-1 downto 1);
            temp1 <= '0'&temp1(n-1 downto 1);
            if count = n-1 then
              n_s <= in_temp1_out_temp2;
              sel <= '0'; -- mux temp2(0) to output
              count := 0;
            else
              sel <= '1'; -- mux temp1(0) to output
              count := count + 1;
            end if;
          when others => null;
        end case;
      end if;
    end if;
  end process;

```

```

-- output multiplexor
process(sel, temp1(0), temp2(0))
begin
if sel = '0' then z <= temp2(0); else
z <= temp1(0);
end if;
end process;

end Behavioral;

-----

-- test bench n = 4
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity double_buffer_tb is
port (ck, btn0, btn1, reset : in std_logic;
      x: in std_logic;
      z: out std_logic;
      z1: out std_logic_vector(3 downto 0);
      z2: out std_logic_vector(3 downto 0);
      t1, t2: out std_logic);
end double_buffer_tb;
architecture struc of double_buffer_tb is
signal en: std_logic;
component double_buffer
generic(n : natural);
port (ck, reset : in std_logic;
      x: in std_logic;
      z: out std_logic;
      z1: out std_logic_vector(n-1 downto 0);
      z2: out std_logic_vector(n-1 downto 0);
      t1, t2: out std_logic);
end component;
begin
dut: double_buffer generic map (4)
port map(en, reset, x, z, z1, z2, t1, t2);

```

```

-- single step, debounce (db)
-- btn0 to enter and btn1 to reset
process(ck)
type db_state is (not_rdy, rdy, pulse);
variable db_ns: db_state;
begin
if ck='1' and ck'event then
    case db_ns is
        when not_rdy => en <= '0';
        if btn1 = '1' then db_ns := rdy; end if;
        when rdy => en <= '0';
        if btn0 = '1' then db_ns := pulse; end if;
        when pulse => en <= '1';
        db_ns := not_rdy;
        when others => null;
    end case;
end if;
end process;
end struc;

```