



Solutions to Digital System Projects Final Practice Problems

By Prawat Nagvajara

Problem 1

```
-- Problem 1. Design an up/down counter
-- using arith and unsigned package
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_signed.all;
entity counter is
    generic ( N: natural := 4);
    port (ck, reset, up_down: in std_logic;
          z : out std_logic_vector(n-1 downto 0)
        );
end counter;
architecture beh of counter is
    signal temp: std_logic_vector(n-1 downto 0);
begin
    process(ck)
    begin
        if ck='1' and ck'event then
            if reset = '1' then
                temp <= (others => '0');
            else
                if up_down = '0' then
                    temp <= temp + 1;
                else
                    temp <= temp - 1;
                end if;
            end if;
        end if;
    end process;
    z <= temp;
end beh;
```

 


Fig. 1 Simulation Wave

Figure 1 shows simulation wave of the up/down counter where the contents of the counter turns over from “0000” to “1111” = -1 when it is counting down.

Problem 2 Up-down counter IP from IP Catalog

 


Fig. 2 Up Down Counter IP Schematic (4-bit)

```
-----
-- Company: Drexel ECE
-- Engineer: Prawat
-- IP Catalog binary counter
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity updown_count is
port( CK, updown : IN STD_LOGIC;
Q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
end updown_count;

architecture Behavioral of updown_count is
COMPONENT c_counter_binary_0
  PORT (
    CLK : IN STD_LOGIC;
    UP : IN STD_LOGIC;
    Q : OUT STD_LOGIC_VECTOR(3 DOWNTO 0)
  );
END COMPONENT;
begin
U : c_counter_binary_0
PORT MAP (CLK => CK,UP => UPdown,Q => Q);
end Behavioral;
```

 


Fig. 3 Up Down Counter Wave

Problem 3

Write a test bench for the factorial sequential circuit for $n = 1, \dots, 10$

Factorial sequential calculator code

```
-----  
-- Factorial Sequential Calculator  
-- After a reset each clock cycle n,  
-- n = 1, 2, ... the output is n!  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use ieee.std_logic_arith.all;  
use ieee.std_logic_unsigned.all;  
entity fact is  
generic (K: natural := 32); -- K number of bits  
port (ck, reset: in std_logic;  
      LED: out std_logic_vector(K-1 downto 0));  
end fact;  
  
architecture Behavioral of fact is  
signal temp: std_logic_vector(2*K - 1 downto 0);  
signal n: std_logic_vector(K-1 downto 0);  
  
begin  
process (ck)  
begin  
if ck='1' and ck'event then  
    if reset = '1' then  
        -- initialize to vector "00..01"  
        temp <= (0=>'1',others=>'0');  
        n <= (0=>'1',others=>'0');  
    else  
        -- K by K product is 2K bits  
        temp <= n * temp(K-1 downto 0);  
        n <= n+1;  
    end if;  
end if;  
end process;  
led <= temp(K-1 downto 0); -- K-bit data  
end Behavioral;
```

```

-----
-- factorial circuit test bench
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity fact_tb is
end fact_tb;
architecture Beh of fact_tb is
component fact
generic (K: natural := 32);--K number of bits
port(ck, reset: in std_logic;
      LED: out std_logic_vector(K-1 downto 0));
end component;
signal z: std_logic_vector(31 downto 0);
signal n, n_factorial: integer := 1;
signal ck: std_logic := '1';
type my_state is (init,run_test,done);
signal n_s: my_state := init;
signal reset: std_logic := '1';
begin
ck <= not ck after 5 ns;
dut: fact generic map(32)
port map(ck, reset, z);

process(ck)
variable n, n_factorial: integer := 0;
begin
if ck = '1' then
case n_s is
when init => reset <= '1';
n := 1;
n_factorial := 1;
n_s <= run_test;
when run_test => reset <= '0';
n_factorial := n*n_factorial;
n := n + 1;
assert conv_integer(unsigned(z)) = n_factorial
report "incorrect" severity ERROR;
if n > 11 then
n_s <= done;
end if;
when done => assert FALSE
report "test completed" severity FAILURE;
end case;
end if;
end process;
end beh;

```

 


Fig. 4 Factorial Test Bench Wave

Problem 4

```
-- Problem 4 Design a combinational block to add
-- two N-digit decimal numbers x and y and
-- implement on FPGA for N = 2.
library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_unsigned.all;
entity decimal_N_digit_add is
generic(N: natural := 3);
port ( x, y : in std_logic_vector(4*N - 1 downto 0);
      z: out std_logic_vector(4*N - 1 downto 0)
);
end decimal_N_digit_add;

architecture beh of decimal_N_digit_add is
begin
process(x,y)
variable carry: std_logic;
variable temp, temp_x, temp_y: std_logic_vector(4 downto 0);
begin
-- reset carry
carry := '0';
for i in 0 to N-1 loop
temp_x := '0' & x(4*(i+1)-1 downto 4*i);
temp_y := '0' & y(4*(i+1)-1 downto 4*i);
temp := temp_x + temp_y;
if carry = '1' then
temp := temp + 1;
end if;
if temp > 9 then
carry := '1';
temp := temp + 6;
end if;
-- assign temp to output
z(4*(i+1)-1 downto 4*i) <= temp(3 downto 0);
end loop;
end process;
end beh;
```

/decimal_n_digit_add/x	710	693	583	710
/decimal_n_digit_add/y	098	297	682	098
/decimal_n_digit_add/z	808	990	265	808

Fig. 5 Decimal N-digit Adder

Problem 5

```
-- Problem 5 Design a signed accumulator similar to
-- the IP catalog core with generic parameters,
-- n-bit data and L clock-cycles latency.
-- Use a shift register with depth L-1 to buffer
-- the input data to emulate the latency.

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;
use ieee.std_logic_signed.all;

entity accumulator_latency_L is
generic( N: natural := 4;
        L: natural := 3);
port (ck, reset : in std_logic;
      x : in  std_logic_vector(n-1 downto 0);
      z : out std_logic_vector(2*n-1 downto 0)
    );
end accumulator_latency_L;

architecture beh of accumulator_latency_L is
type vector_array is
array (natural range <>) of std_logic_vector(n-1 downto 0);
signal latency_temp: vector_array(0 to L-2);
signal zero_vector, one_vector: std_logic_vector(n-1 downto 0);
signal temp, temp_x: std_logic_vector(2*n-1 downto 0);
begin
```

	clk	reset	x	z	latency_temp	temp_x	temp	zero_vector	one_vector
	1	1	7	0	{0} {0}	0	0	0	-1
			-1	5	{7} {0}	7	7		
			-3	3	{-1} {7}	-1	7		
			6	11	{5} {-1}	5	11		
			7	8	{-3} {5}	-3	8		
			-2	11	{3} {-3}	6	11		
			0	17	{6} {3}	7	17		
				24	{7} {6}	-2	24		
				22	{-2} {7}	0	22		
					{0} {-2}				
					{0} {0}				

Fig. 6 Accumulator Simulation Wave