



Array Calculating Absolute Value of a Signed Vector

By Prawat Nagvajara

Synopsis

This note covers an array structure for calculating the absolute value of a signed n-bit vector.

Code

The code first constructs the processing element which adds the not x and c_in. Next, the two's complement array comprises the processing elements where the rightmost cell has a one as c_in, effectively, adding a one to the one's complement of x. Figure 1 shows a schematic of the array.

 


Fig. 1 Two's Complement Array

A multiplexer selects x or the two's complement of x to the output z based on the leftmost bit x(n-1) of the input x. This follows from the fact that a signed number is negative if and only if the leftmost bit is a one.

```
-----  
-- Company: Drexel ECE  
-- Engineer: Prawat  
-- Description: Absolute value circuit comprises  
-- processing elements calculating the two's  
-- complement. The output is the two's complement  
-- of the input if the input is negative.  
-----  
  
-----  
-- processing element  
-- Adding two bits x and c_in  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity pe is  
    port (x, c_in : in std_logic;  
          z, c_out : out std_logic);  
end pe;  
architecture dataflow of pe is  
begin  
    c_out <= (not x) and c_in;  
    z <= (not x) xor c_in;  
end dataflow;  
  
-----  
-- Absolute Array  
-- Array calculating the two's complement  
-- A mux assigning the output  
-- if x<0 then z <= -x; else z <= x; end if;  
-----  
  
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
entity abs_array is  
    generic (n: natural := 4);  
    port (x : in std_logic_vector(n-1 downto 0);  
          z : out std_logic_vector(n-1 downto 0));  
end abs_array;  
  
architecture Behavioral of abs_array is  
    component pe is  
        port (x, c_in : in std_logic;  
              z, c_out : out std_logic);  
    end component;  
    signal c,w: std_logic_vector(n-1 downto 0);
```

```

begin
-----
-- array calculating -x
-----
c(0) <= '1';
G1: for i in 0 to n-1 generate
G2: if i < n-1 generate
U: pe port map(x(i), c(i), w(i), c(i+1));
end generate G2;
G3: if i = n-1 generate
U: pe port map(x(i), c(i), w(i), open);
end generate G3;
end generate G1;
-----
-- mux
-----
process(x(n-1), w)
begin
  if x(n-1) = '1' then z <= w;
  else z <= x;
  end if;
end process;
end Behavioral;

```

Verification

Figure 2 below shows a simulation wave. The number of bits n is default to 4. When the input x is negative the output z is the two's complement of x . When x is equal to -2^{n-1} the output is incorrect because the correct result positive 2^{n-1} requires at least $n+1$ bits as for its representation. For instance, the two's complement of -4 ("1100") is 4 ("0100"), however, with the 3-bit representation -4 is "100" however positive 4 cannot be presented with a 3-bit vector.

/x	1100	1101	0101	1001	1011	1111	0001	1000	1100
/c	0111	0001						1111	0111
/w	0100	0011	1011	0111	0101	0001	1111	1000	0100
/z	0100	0011	0101	0111	0101	0001		1000	0100

Fig. 2 Simulation Wave