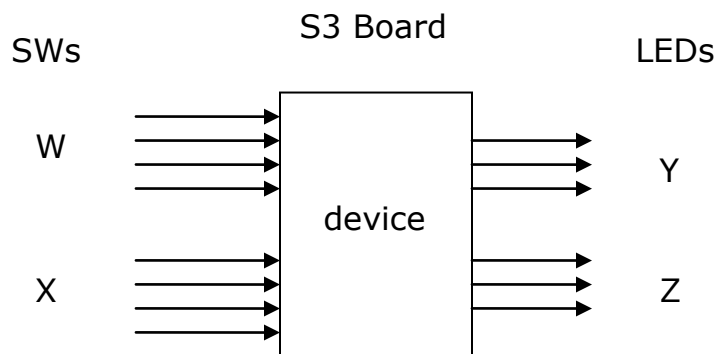




Electrical and Computer Engineering  
ECE-C302

### Quiz 1

Implement a combinational device whose outputs Y and Z are 3-bit vectors representing integers range 0 to 7. The output Y is equal to the number of cases when both inputs W(i) and X(i) for  $i = 0, \dots, 3$ , are a one. And the output Z is the number of cases W(i) and X(i) are both zero.



Entity device is

```
Port (W, X : in std_logic_vector(0 to 3);
```

```
      Y, Z : out std_logic_vector(2 downto 0));
```

```
End device;
```

```
Architecture ...
```

```
-- W(i) = X(i) and W(i) = '1' then count
```

```
variable count1, count0 : integer;
```

```
begin
```

```
count1 := 0; count0 := 0;
```

```
for I in 0 to 3 loop
```

```
if W(i) = X(i) and W(i) = '1' then count1 := count1 + 1; end if;
```

```
end loop;
```

```
case count1 is
```

```
when 0 => y <= "000";
```

```
...
```

```
-- the same for counting '0' match.
```

```
for I in 0 to 3 loop
```

```
if W(i) = X(i) and W(i) = '0' then count0 := count0 + 1; end if;
```

```
end loop;
```