




Electrical and Computer Engineering

ECE-C302

Quiz 1

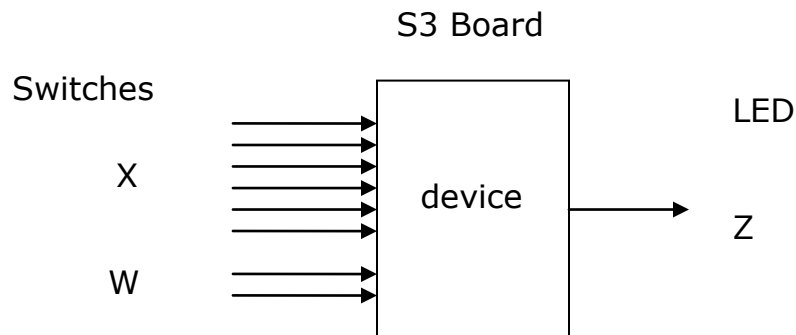Implement a combinational circuit with 6-bit input X. W is a select 2-bit input ranging from 0 to 3, i.e., "00", "01", "10", "11". The output Z is a one if the number of one's appearing at the input is greater than W.



Entity Q1 is

```
Port (X : in std_logic_vector(0 to 5);  
      w : in std_logic_vector(1 downto 0);  
      Z: out std_logic);
```

End Q1;

Architecture beh of q1 is

Begin

Process(x, w)

Variable count : integer;

Begin

Count := 0;

For I in 0 to 5 loop

If x(i) = '1' then count := count + 1; end if;

End loop;

Case w is

When "00" => if count > 0 then z <= '1'; else Z <= '0'; end if;

When "01" => if count > 1 then z <= '1'; else Z <= '0'; end if;

When "10" => if count > 2 then z <= '1'; else Z <= '0'; end if;

When "11" => if count > 3 then z <= '1'; else Z <= '0'; end if;

End case;

End process;

End beh;