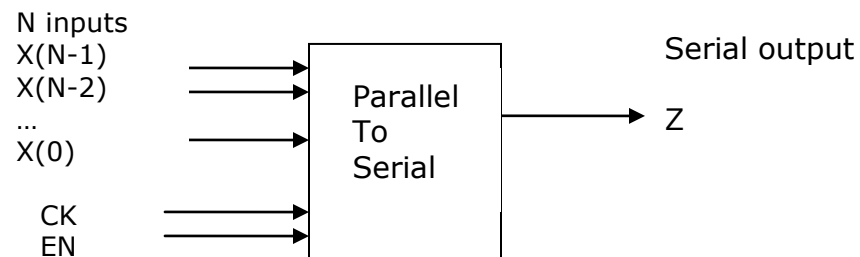




Electrical and Computer Engineering
ECE-C302

Quiz 2



Entity p2s is

Generic (N : natural := 4);


Port (X : in std_logic_vector(N-1 downto 0);

CK, EN : in std_logic;

Z : out std_logic);

End p2s;

 In converting parallel input data to serial data for transmission the device loads the input vector X into its internal register every N clock-cycles period. The device serially outputs $X(0)$, $X(1)$, ..., $X(N-1)$ at each clock rising edge. The figure below shows a plausible design based on internal shift-register with parallel load and shift enables.



$X(0)$ appears at the output Z after EN changes from zero to one and $X(1)$, ..., $X(N-1)$ on the following clock cycles. EN must remain a one at all time during the transmission. The new $X(0)$ appears at the output Z the cycle after the old $X(N-1)$. The output port Z is a zero when En is a zero.

Design and show the correctness by running simulation for $N = 4$.

Hint: For $N=2$ the internal register loads and shifts on the alternate clock cycles, and for $N=3$ the register loads followed by 2 shifts, periodically.

-- A Sketch

Architecture beh of p2s is

```

Type my_state is (idle, load, shift);
Signal n_s : my_state;
Signal temp: std_logic_vector(N-1 downto 0); -- place holder
Signal count : integer;
Begin
Z <= temp(0); -- wire to output
Process(ck)
Begin
If ck='1' and ck'event then
  If en = '0' then n_s <= idle; else
    When idle => if en = '1' then n_s <= load; end if;
                    Count <= 0; temp <= (others => '0'); -- clear register
    When load => temp <= x; count <= count + 1;
                    n_s <= shift;
    When shift => if count = N-1 then n_s <= load; end if;
                    For I in N-1 downto 1 loop -- left shift
                        Temp(i-1) <= temp(i);
                    End loop;
    End case;
  End if;
End if;
End process;
End beh;

```